

# Lab 1: Introduction to git and VHDL

---

## Links

[My github repository](#)

[My EDAPlayground](#)

## Task 1: De Morgan's

Function and truth table

$$f(c, b, a) = \bar{b}a + \bar{c}\bar{b}$$

$$f(c, b, a)_{\text{NAND}} =$$

$$f(c, b, a)_{\text{NOR}} =$$

| c | b | a | f(c,b,a) |
|---|---|---|----------|
| 0 | 0 | 0 | 1        |
| 0 | 0 | 1 | 1        |
| 0 | 1 | 0 | 0        |
| 0 | 1 | 1 | 0        |
| 1 | 0 | 0 | 0        |
| 1 | 0 | 1 | 1        |
| 1 | 1 | 0 | 0        |
| 1 | 1 | 1 | 0        |

De Morgan's source code: Listings of [design.vhd](#)

```

-----
library IEEE;
use IEEE.std_logic_1164.all;
-----
-- Entity declaration for basic gates
-----
entity gates is
    port(
        a_i    : in  std_logic;    -- Data input
        b_i    : in  std_logic;    -- Data input
        c_i    : in  std_logic;    -- Data input
        f_o     : out std_logic;    -- output function
        fnand_o : out std_logic;    -- NAND output function
        fnor_o  : out std_logic;    -- NOR output function
    );

```

```

end entity gates;


-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
    f_o    <= (not(b_i) and a_i) or (not(c_i) and not(b_i));
    fnand_o <= not(not(not(b_i) and a_i) and not(not(c_i) and not(b_i)));
    fnor_o  <= not(b_i or not(a_i)) or not(c_i or b_i);

end architecture dataflow;

```

## Simulated time waveform

 

## Task 2: Distributive law

### Equations

$$x \cdot y + x \cdot z = x \cdot (y + z)$$

$$(x + y) \cdot (x + z) = x + (y \cdot z)$$

It should hold that  $f(x,y,z)=g(x,y,z)$ , where  $f(x,y,z)$  are expressions on the left side of  $=$  and  $g(x,y,z)$  equivalent expressions on the right.

### Listing of `design.vhd`

```

-----
-- Libraries
-----

library IEEE;
use IEEE.std_logic_1164.all;

-----
-- Entity declaration for basic gates
-----

entity gates is
    port(
        x_i    : in  std_logic;    -- Data input
        y_i    : in  std_logic;    -- Data input
        z_i    : in  std_logic;    -- Data input
        f1_o    : out std_logic;    -- original expressions on the left

```

```

        f2_o  : out std_logic;
        g1_o  : out std_logic;      -- equivalent expressions on the right
        g2_o  : out std_logic
    );
end entity gates;

-----
-- Architecture body for basic gates on distributive rule
-- It should hold that f1_o = g1_o and f2_o=g2_o as proof for distr. law
-----

architecture dataflow of gates is
begin
    f1_o  <= (x_i and y_i) or (x_i and z_i);
    g1_o  <= x_i and (y_i or z_i);
    f2_o  <= (x_i or y_i) and (x_i or z_i);
    g2_o  <= x_i or (y_i and z_i);

end architecture dataflow;

```

## Simulated waveform

