


Masauso Lungu 209533

Lab 6: Driver for multiple seven-segment displays

Links:

[My github repository](#)

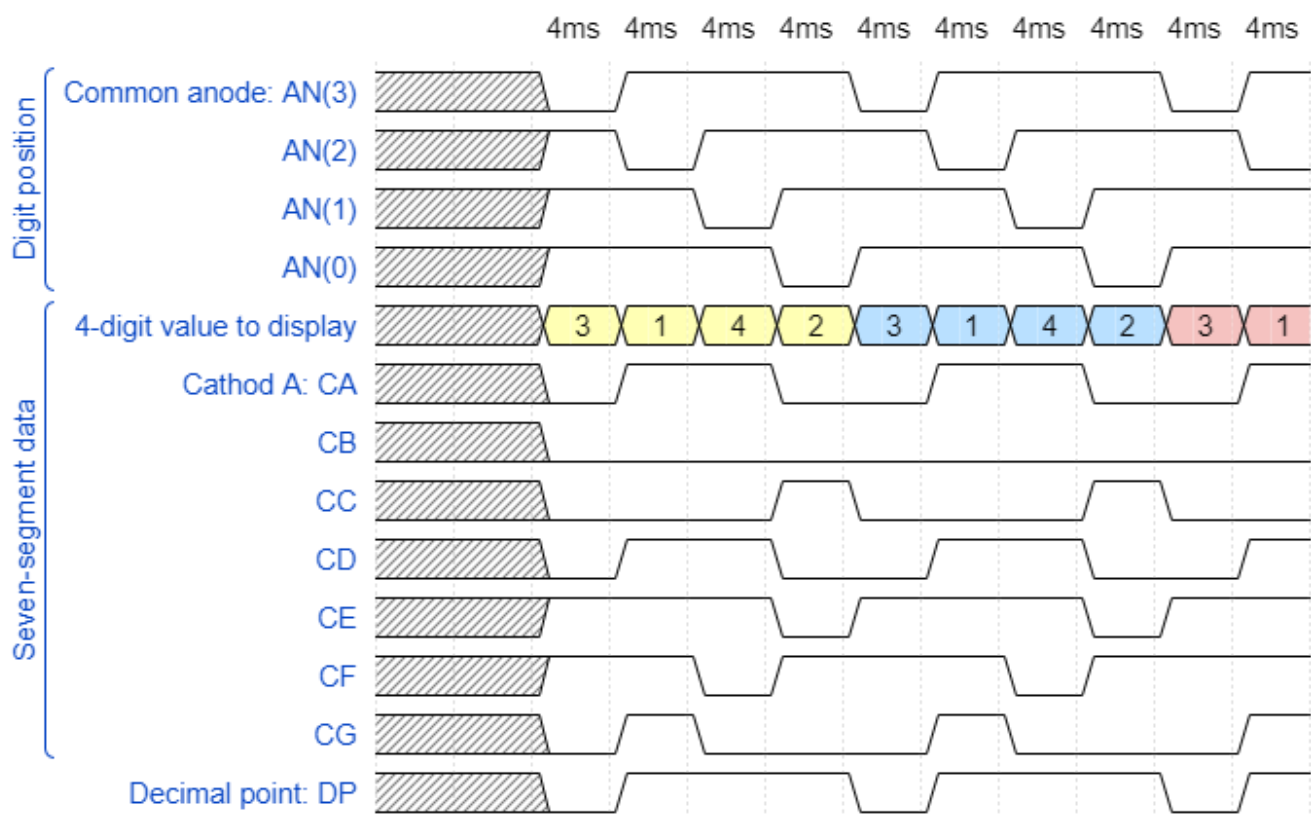1 Preparation tasks (done before the lab at home)



Source code used

```
{
  signal:
  [
    ['Digit position',
      {name: 'Common anode: AN(3)', wave: 'xx01..01..01'},
      {name: 'AN(2)', wave: 'xx101..01..0'},
      {name: 'AN(1)', wave: 'xx1.01..01..'},
      {name: 'AN(0)', wave: 'xx1..01..01.'},
    ],
    ['Seven-segment data',
      {name: '4-digit value to display', wave: 'xx3333555599', data:
```

```
[ '3', '1', '4', '2', '3', '1', '4', '2', '3', '1' ]},
  {name: 'Cathod A: CA', wave: 'xx01.0.1.0.1'},
  {name: 'CB', wave: 'xx0.....'},
  {name: 'CC', wave: 'xx0..10..10.'},
  {name: 'CD', wave: 'xx01.0.1.0.1'},
  {name: 'CE', wave: 'xx1..01..01.'},
  {name: 'CF', wave: 'xx1.01..01..'},
  {name: 'CG', wave: 'xx010..10..1'},
],
{name: 'Decimal point: DP', wave: 'xx01..01..01'},
],
head:
```

2 Display driver

Listing of VHDL code of the process `p_mux`

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
  case s_cnt is
    when "11" =>
      s_hex <= data3_i;
      dp_o  <= dp_i(3);
      dig_o <= "0111";

    when "10" =>
      -- WRITE YOUR CODE HERE
      s_hex <= data2_i;
      dp_o  <= dp_i(2);
      dig_o <= "1011";

    when "01" =>
      -- WRITE YOUR CODE HERE
      s_hex <= data1_i;
      dp_o  <= dp_i(1);
      dig_o <= "1101";

    when others =>
      -- WRITE YOUR CODE HERE
      s_hex <= data0_i;
      dp_o  <= dp_i(0);
      dig_o <= "1110";
  end case;
end process p_mux;

end architecture Behavioral;
```

Listing of VHDL testbench file `tb_driver_7seg_4digits`

```

-----

library ieee;
use ieee.std_logic_1164.all;

-----

-- Entity declaration for testbench
-----

entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;

-----

-- Architecture body for testbench
-----

architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time      := 10 ns;

    --Local signals
    signal s_clk_100MHz : std_logic;
    --- WRITE YOUR CODE HERE
    signal s_clk          : std_logic;
    signal s_reset        : std_logic;
    signal s_data0_i      : std_logic_vector(4 - 1 downto 0);
    signal s_data1_i      : std_logic_vector(4 - 1 downto 0);
    signal s_data2_i      : std_logic_vector(4 - 1 downto 0);
    signal s_data3_i      : std_logic_vector(4 - 1 downto 0);
    signal s_dp_i         : std_logic_vector(4 - 1 downto 0);
    signal s_dp_o         : std_logic;
    signal s_seg_o        : std_logic_vector(7 - 1 downto 0);
    signal s_dig_o        : std_logic_vector(4 - 1 downto 0);

begin
    -- Connecting testbench signals with driver_7seg_4digits entity
    -- (Unit Under Test)
    --- WRITE YOUR CODE HERE
    uut_driver_7seg : entity work.driver_7seg_4digits
        port map(
            clk      => s_clk_100MHz,
            reset    => s_reset,
            data0_i  => s_data0_i,
            data1_i  => s_data1_i,
            data2_i  => s_data2_i,
            data3_i  => s_data3_i,
            dp_i     => s_dp_i,
            dp_o     => s_dp_o,
            seg_o    => s_seg_o,
            dig_o    => s_dig_o
        );

```

```

-- Clock generation process
-----
p_clk_gen : process
begin
    while now < 750 ns loop          -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----

-- Reset generation process
-----
--- WRITE YOUR CODE HERE
p_reset_gen : process
begin
    s_reset <= '0';
    wait for 10 ns;
    s_reset <= '1';
    wait for 50 ns;
    s_reset <= '0';
    wait;
end process p_reset_gen;

-----

-- Data generation process
-----
--- WRITE YOUR CODE HERE
p_stimulus : process
begin
    report "Stimulus process started" severity note;


    s_data3_i <= "0011";
    s_data2_i <= "0001";
    s_data1_i <= "0100";
    s_data0_i <= "0010";
    s_dp_i    <= "0111";

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

end architecture testbench;

```

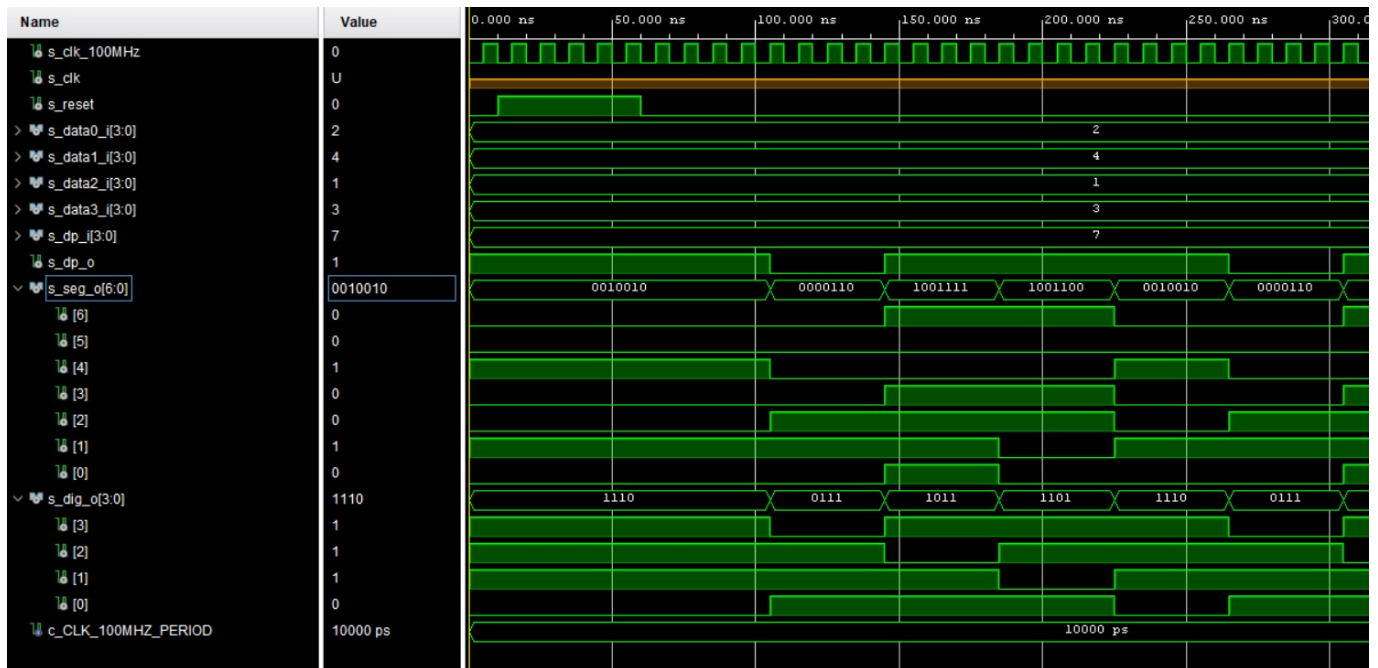Screenshot with simulated time waveforms;



Listing of VHDL architecture of the top layer

```

architecture Behavioral of top is
    -- No internal signals
begin

    -----

    -- Instance (copy) of driver_7seg_4digits entity
    driver_seg_4 : entity work.driver_7seg_4digits
        port map(
            clk          => CLK100MHZ,
            reset        => BTNC,
            data0_i(3)   => SW(3),
            data0_i(2)   => SW(2),
            data0_i(1)   => SW(1),
            data0_i(0)   => SW(0),
            --- WRITE YOUR CODE HERE
            data1_i(3)   => SW(7),
            data1_i(2)   => SW(6),
            data1_i(1)   => SW(5),
            data1_i(0)   => SW(4),

            data2_i(3)   => SW(11),
            data2_i(2)   => SW(10),
            data2_i(1)   => SW(9),
            data2_i(0)   => SW(8),

            data3_i(3)   => SW(15),
            data3_i(2)   => SW(14),
            data3_i(1)   => SW(13),
            data3_i(0)   => SW(12),

            dp_i  => "0111",

```

```
        dig_o => AN(3 downto 0),

        seg_o(0) => CA,
        seg_o(1) => CB,
        seg_o(2) => CC,
        seg_o(3) => CD,
        seg_o(4) => CE,
        seg_o(5) => CF,
        seg_o(6) => CG,
        dp_o    => DP

    );

    -- Disconnect the top four digits of the 7-segment display
    AN(7 downto 4) <= b"1111";

end Behavioral;
```

3. Eight-digit driver

