

Lab 2: Combinational Logics

Preparation tasks

Digital or Binary comparator compares the digital signals A, B presented at input terminal and produce outputs depending upon the condition of those inputs. Complete the truth table for 2-bit *Identity comparator* (B equals A), and two *Magnitude comparators* (B is greater than A, B is less than A). Note that, such a digital device has four inputs and three outputs/functions.

Dec. equivalent	B[1:0]	A[1:0]	B is greater than A	B equals A	B is less than A
0	0 0	0 0	0	1	0
1	0 0	0 1	0	0	1
2	0 0	1 0	0	0	1
3	0 0	1 1	0	0	1
4	0 1	0 0	1	0	0
5	0 1	0 1	0	1	0
6	0 1	1 0	0	0	1
7	0 1	1 1	0	0	1
8	1 0	0 0	1	0	0
9	1 0	0 1	1	0	0
10	1 0	1 0	0	1	0
11	1 0	1 1	0	0	1
12	1 1	0 0	1	0	0
13	1 1	0 1	1	0	0
14	1 1	1 0	1	0	0
15	1 1	1 1	0	1	0